

ש'טן מ'עוילען א פ'סען א'רעכענען א'רשט:

$$(1) \quad \tilde{V}_1 = j5\tilde{I}_1 + j20 \cdot \tilde{I}_2$$

$$(2) \quad \tilde{V}_2 = j 20 \tilde{I}_1 + j 125 \tilde{I}_2$$

מ'ס' קל 11 חזקת נאמנות : משנה

$$(3) \quad 425 \angle 0^\circ - 5 \tilde{I}_1 - \tilde{V}_1 = 0$$

מסמלואי טורו דפוליי עמא ע'ס' ג' צ' ו'ס' ג' א' פ' .

צדקה יום שבת

$$\begin{cases} \tilde{V}_{out} = \tilde{V}_2 + 45\tilde{I}_2 \\ \tilde{I}_2 = 0 \end{cases}$$

$$\tilde{V}_{\text{out}} = \tilde{V}_{\text{out}}^{\text{II}} = \tilde{V}_2$$

30 103 N_y (1) (3) 51 kN 2 $I_2 = 0$ 2' 3_y

$$: \vec{V}_1, \vec{V}_2, \vec{F}_1$$

$$\begin{cases} \tilde{V}_1 = 212.5 + 215.5j \\ \tilde{V}_2 = 850 + 850j \\ \tilde{I}_1 = 42.5 - 42.5j \end{cases}$$

$$\tilde{V}_{\circ c} = \tilde{V}_2$$

: 3q + 10'5 nly

$$(4) \quad 0 = \tilde{V}_{out} = \tilde{V}_2 + 45\tilde{I}_2$$


• p' nly 4 → 4' nly 4
: \tilde{I}_2 5' 10' 3' nly 4' nly 4' nly


$$\tilde{I}_{sc} = -\tilde{I}_2 \quad \text{oln" 4' nly 4' nly}$$

$$\begin{cases} \tilde{I}_1 = 62.5 - 22.5j \\ \tilde{I}_2 = -10 \\ \tilde{V}_1 = 112.5 + 112.5j \\ \tilde{V}_2 = 450 \end{cases}$$

$$\tilde{I}_{sc} = 10$$

: 1' 5' 0' nly

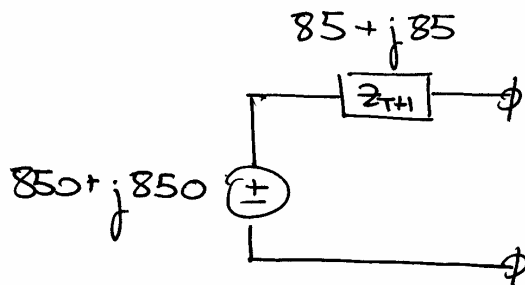

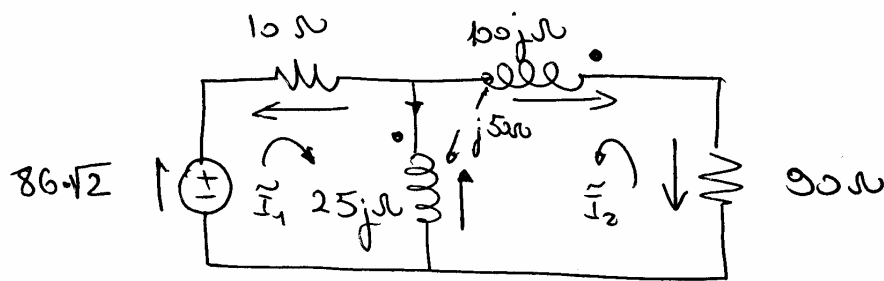

$$0.8 = k = \frac{|M|}{\sqrt{L_1 L_2}} \Rightarrow |M| = 0.8 \sqrt{L_1 L_2} = 0.01$$

$$\Rightarrow j\omega M = j50 \Omega$$

2100 \rightarrow 100 \rightarrow kvl \rightarrow 1111111

$$\begin{cases} 86\sqrt{2} - 10\tilde{I}_1 - (25j(\tilde{I}_1 + \tilde{I}_2) + j50\tilde{I}_2) = 0 \\ [25j(\tilde{I}_1 + \tilde{I}_2) + j50\tilde{I}_2] + [100j\tilde{I}_2 + 50j(\tilde{I}_1 + \tilde{I}_2)] + 90\tilde{I}_2 = 0 \end{cases}$$

\tilde{I}_1, \tilde{I}_2 1.3 V 100 V


$$\begin{cases} \tilde{I}_1 \approx 6.31 - j1.17 \\ \tilde{I}_2 \approx -1.94 - j0.39 \end{cases}$$

$$\tilde{V}_R = \tilde{I}_2 \cdot R \approx -174 - 35.1j$$

100 V

$$V_{R, RMS} = \frac{|\tilde{V}_R|}{\sqrt{2}} \approx 126 V$$

$$P_R = \frac{|\tilde{V}_R|^2}{2R} \approx 176 W$$

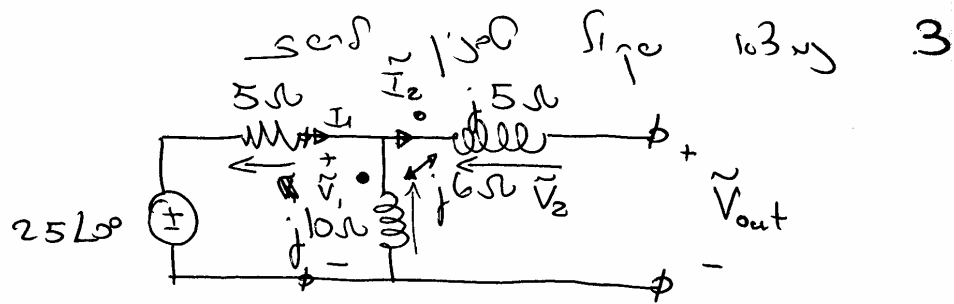

1. 25V DC source is active, 15V AC source is inactive

$$(1) \quad \tilde{V}_1 = j10(\tilde{I}_1 - \tilde{I}_2) + j6 \cdot \tilde{I}_2$$

$$(2) \quad \tilde{V}_2 = j5 \cdot \tilde{I}_2 + j6(\tilde{I}_1 - \tilde{I}_2)$$

2. 15V AC source is active, 25V DC source is inactive

$$(3) \quad 25\angle 0^\circ - 5\tilde{I}_1 - \tilde{V}_1 = 0$$

3. 15V AC source is active, 25V DC source is inactive

$$(4) \quad \tilde{V}_1 = \tilde{V}_2$$

$$\tilde{I}_{sc} = \tilde{I}_2$$

$$\tilde{I}_2 = 5\angle 135^\circ$$

4. 25V DC source is active, 15V AC source is inactive


$$(4') \quad \tilde{I}_2 = 0$$

$$\tilde{V}_{oc} = \tilde{V}_1 - \tilde{V}_2$$

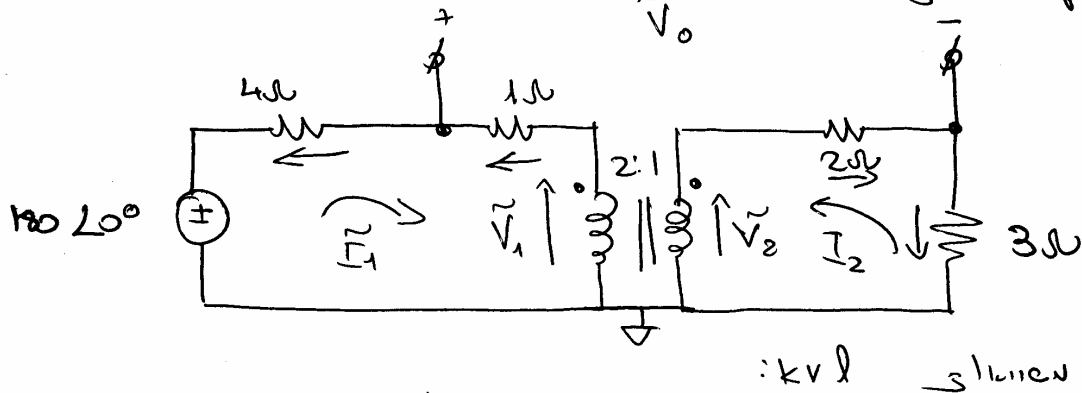5. 25V DC source is active, 15V AC source is inactive

$$Z_L = 10\Omega$$

$R_L = 1 \Omega$ $V = 10 \angle 0^\circ$ $S_{pe} = 1.3 \text{ W}$ 4



$$\begin{cases} 180 \angle 0^\circ - 4\tilde{I}_1 - \tilde{V}_1 - \tilde{V}_2 = 0 \\ \tilde{V}_2 + 2\tilde{I}_2 + 3\tilde{I}_2 = 0 \end{cases}$$

transformer relations


$$\begin{cases} \tilde{V}_2 = \frac{1}{2}\tilde{V}_1 \\ \tilde{I}_2 = -2\tilde{I}_1 \end{cases}$$

$\tilde{V}_1, \tilde{V}_2, \tilde{I}_1, \tilde{I}_2$ unknowns 4

$$\tilde{V}_{oo} = V_+ - V_- = \underbrace{(180 - 4\tilde{I}_1)}_{V_+} - \underbrace{(-3\tilde{I}_2)}_{V_-}$$

$$\tilde{V}_{oo} = 108 \angle 0^\circ$$

result

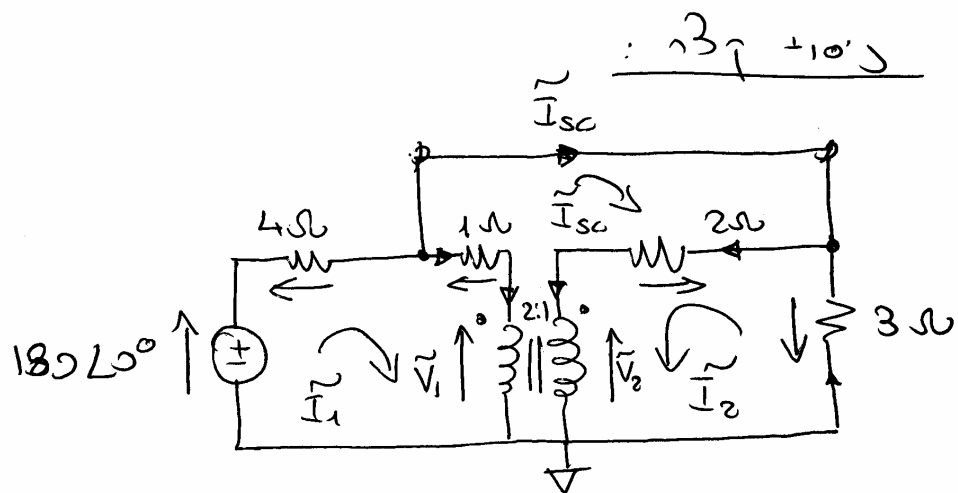

: KVL \rightarrow KVL

$$\text{1. KVL} \quad 180 \angle 0^\circ - 4\tilde{I}_1 - 1(\tilde{I}_1 - \tilde{I}_{sc}) - \tilde{V}_1 = 0$$

$$\text{2. KVL} \quad \tilde{V}_2 + 2(\tilde{I}_2 + \tilde{I}_{sc}) + 3\tilde{I}_2 = 0$$

$$\text{3. KVL} \quad \tilde{V}_1 + 1(\tilde{I}_1 - \tilde{I}_{sc}) - 2(\tilde{I}_2 + \tilde{I}_{sc}) - \tilde{V}_2 = 0$$

: KVL \rightarrow KVL

$$\begin{cases} \tilde{V}_2 = \frac{1}{2} \tilde{V}_1 \\ (\tilde{I}_1 - \tilde{I}_{sc}) = -2(\tilde{I}_2 + \tilde{I}_{sc}) \end{cases}$$


Step 2: Find V_{TH} and Z_{TH}

$$V_{TH} = 18 \angle 0^\circ$$

$$Z_{TH} = 2 \angle 180^\circ$$

$$Z_{SC} = 5 \angle 0^\circ$$

Find V_{TH} and Z_{TH}

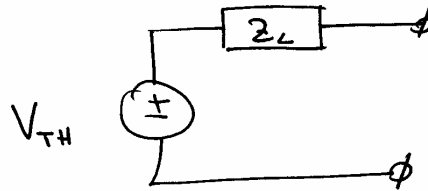


$$V_{TH} = 108 \angle 0^\circ$$

$$Z_{TH} = 2 \Omega$$

or

$$R_L = 2 \Omega$$

.5

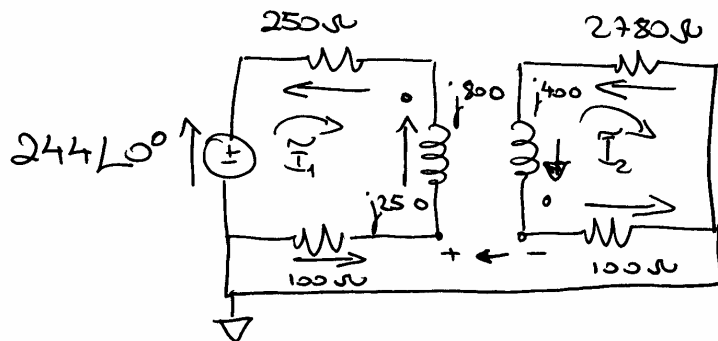

:kvl

$$\begin{cases} 244 - 250\tilde{I}_1 - [j250\tilde{I}_1 + j800\tilde{I}_2] - 100\tilde{I}_1 = 0 \\ [j400\tilde{I}_2 + j800\tilde{I}_1] + 2780\tilde{I}_2 + 100\tilde{I}_2 = 0 \end{cases}$$

:S S21N 21111111 1750

$$\begin{cases} \tilde{I}_1 = 0.637 - j0.053 \\ \tilde{I}_2 = -0.175 - j0.0095 \end{cases}$$

$$\begin{aligned} \tilde{V} = V_+ - V_- &= 100\tilde{I}_1 - (-100\tilde{I}_2) = \\ &= 46.15 - 6.31j \end{aligned}$$